

UNIT 4

Analog and Digital Electronics





Sequential Circuit

Asynchronous Counter

Rajeev Pandey
ECE Department

Asynchronous counter

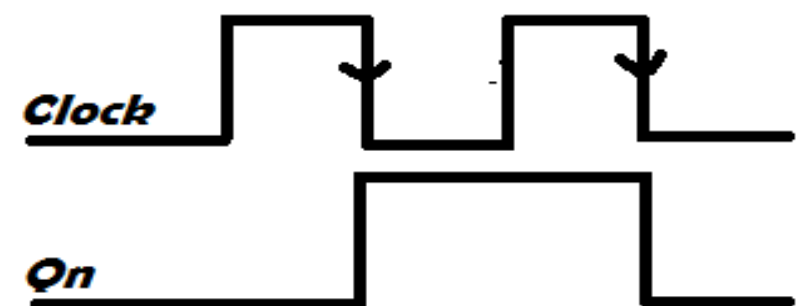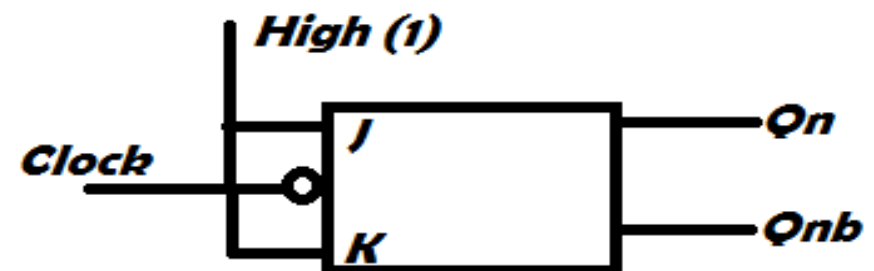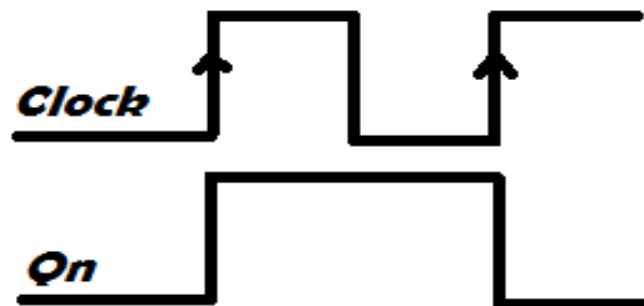
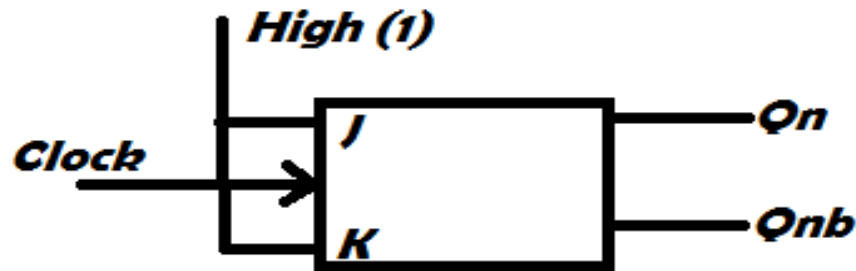
- Output of the first clock act as the clock for the next one.
- T flip-flop or the toggling behaviour of JK Flip is used. At $J=K=1$
- Counter can be Positive edge trigger or negative edge Trigger means it can change its state only at the edge of the clock.



Contd.

- An n -bit counter
- – has n Flip-Flops
- – can cycle through at most 2^n
- Suppose a counter counts
 $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$ ($00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00$) (Two bit & MOD 4 Counter and UP counter)


Initially

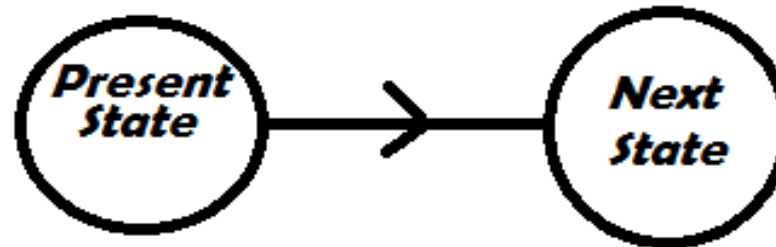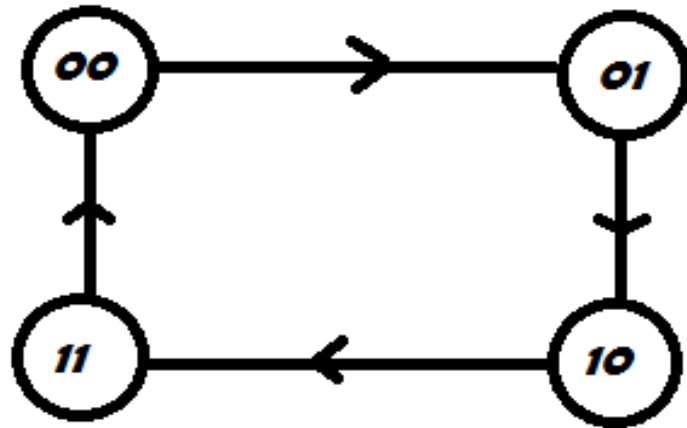

Contd.


Down Counter

Initially

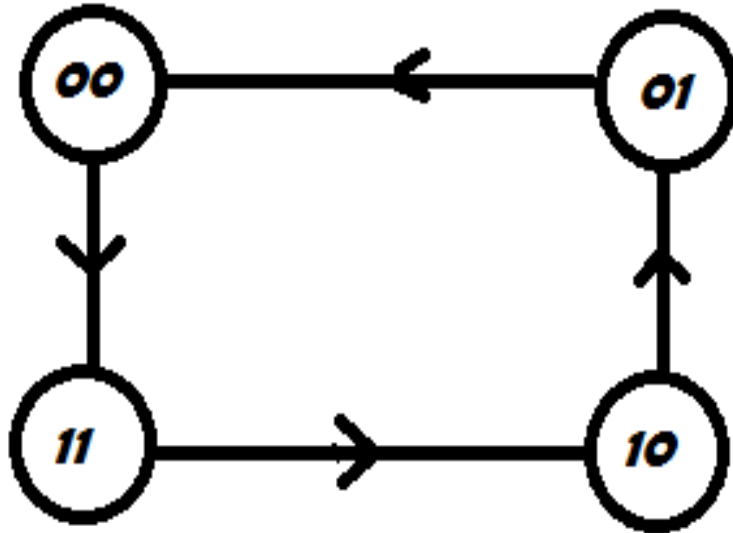

UP and Down Counter


Initially

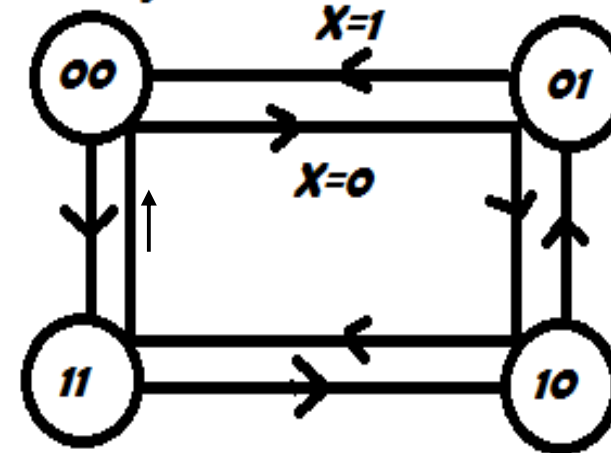


*If control input
 $X=0$ counter act as
UP Counter*

*If the control input
 $X=1$ counter act as
Down counter*

Two bit Asynchronous Counter

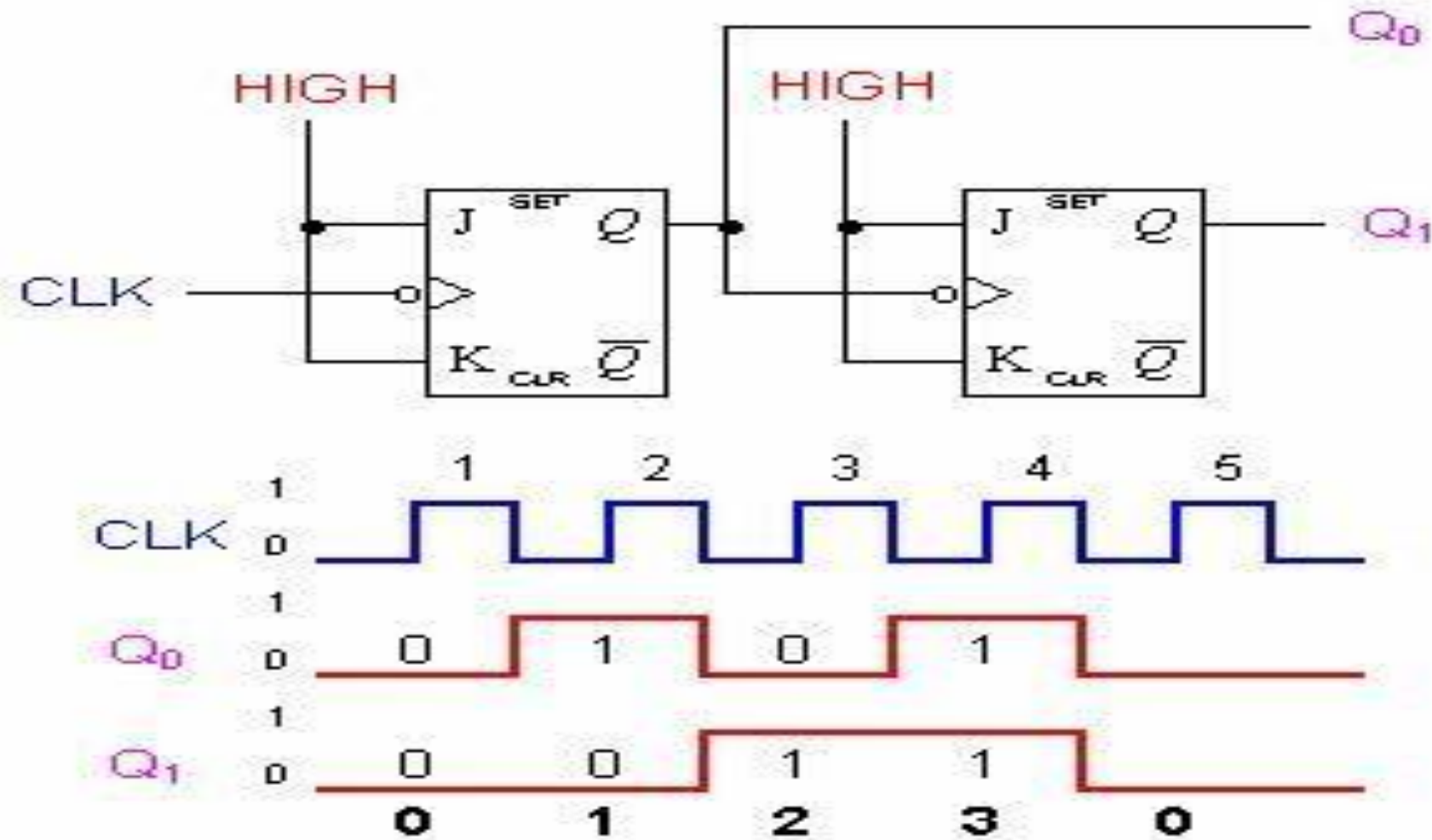


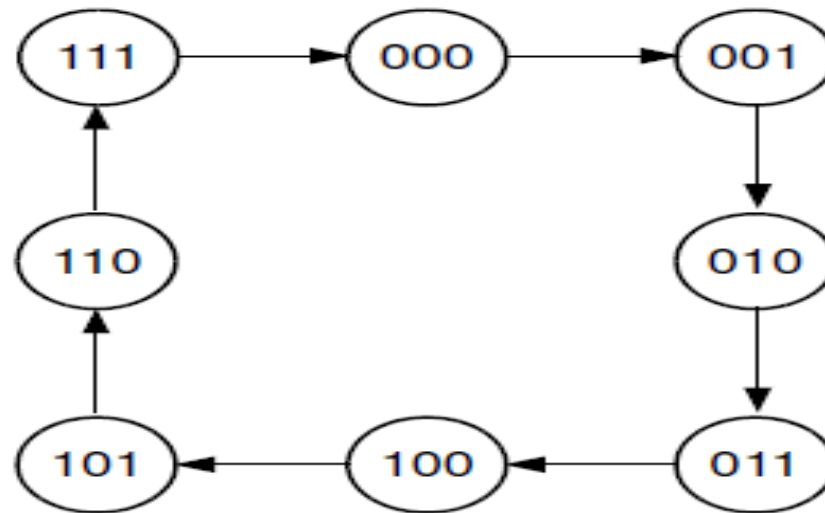Contd. 3 bit counter mod 8 counter
Number of Flip flop require ??




3-bit Counter

Three-bit asynchronous counter

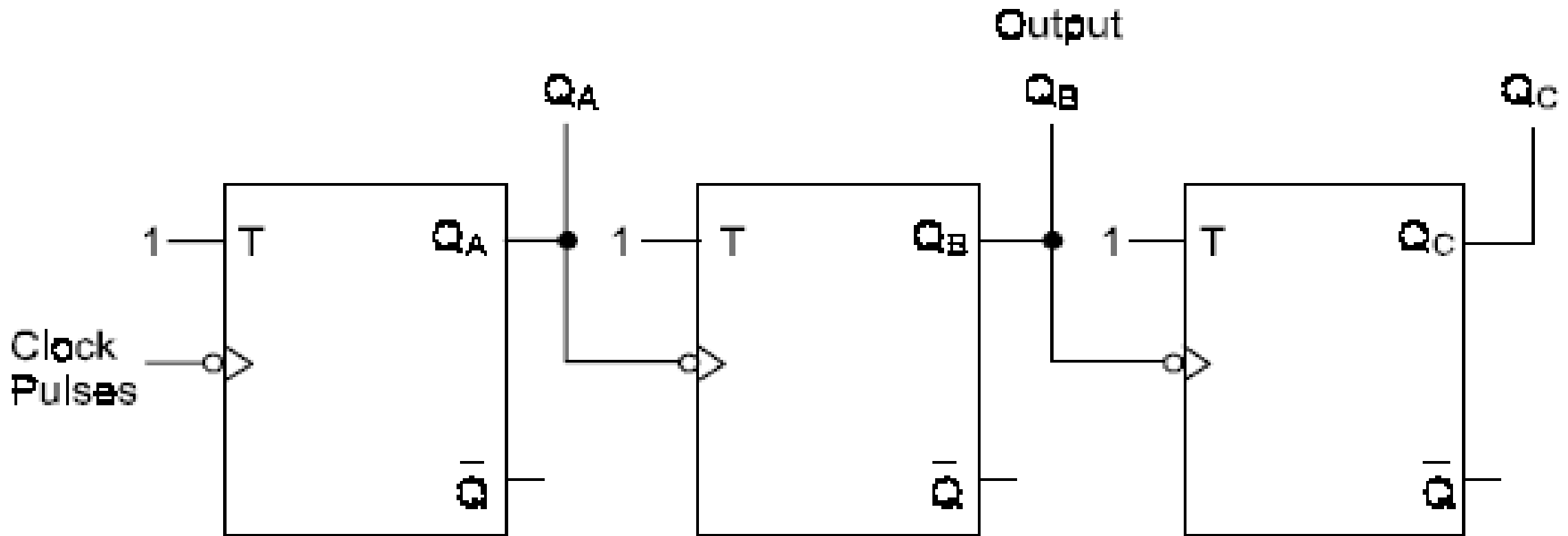


UP counter


UP Counter Output Wave Form

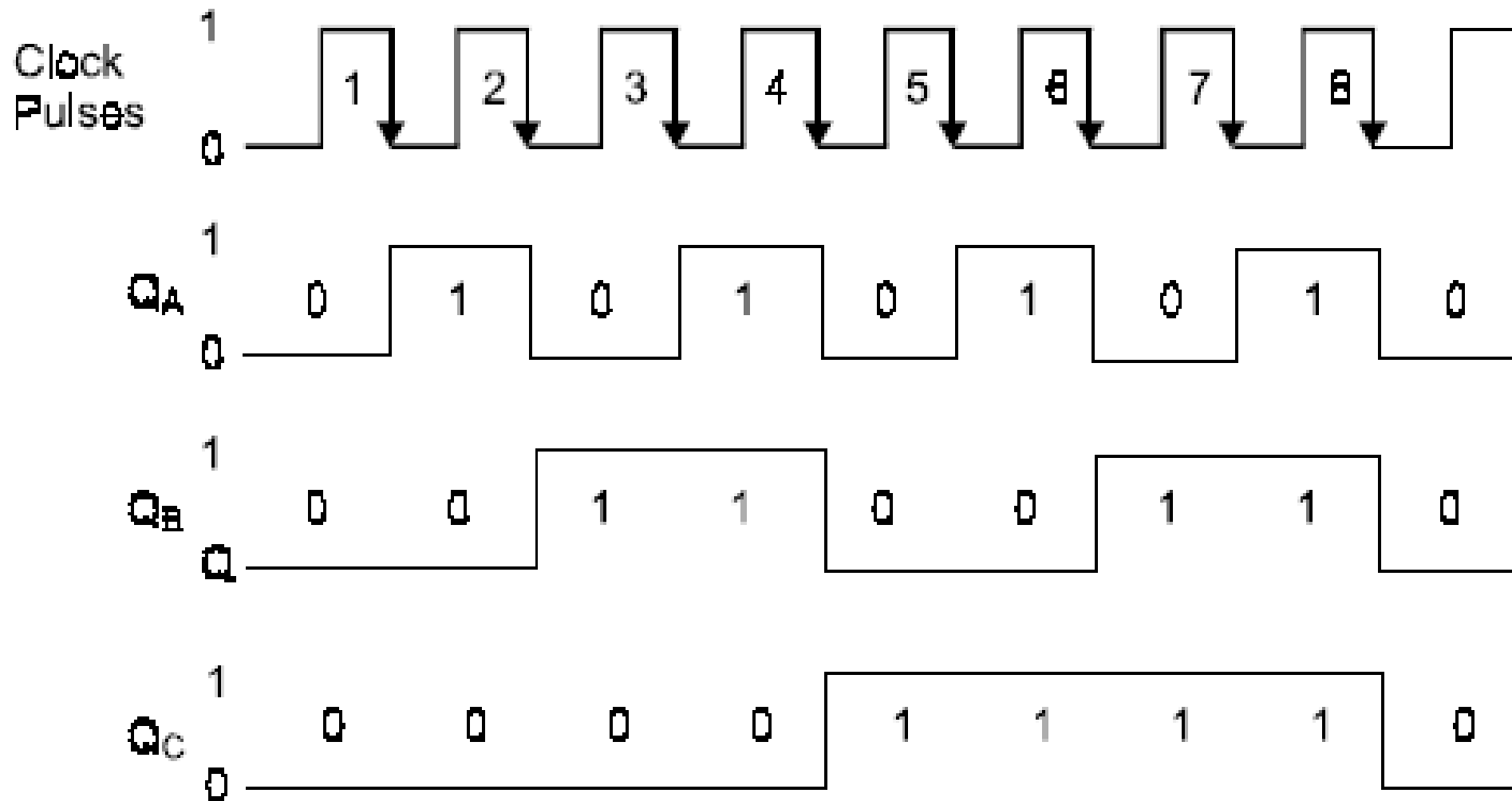


Three-bit asynchronous UP counter

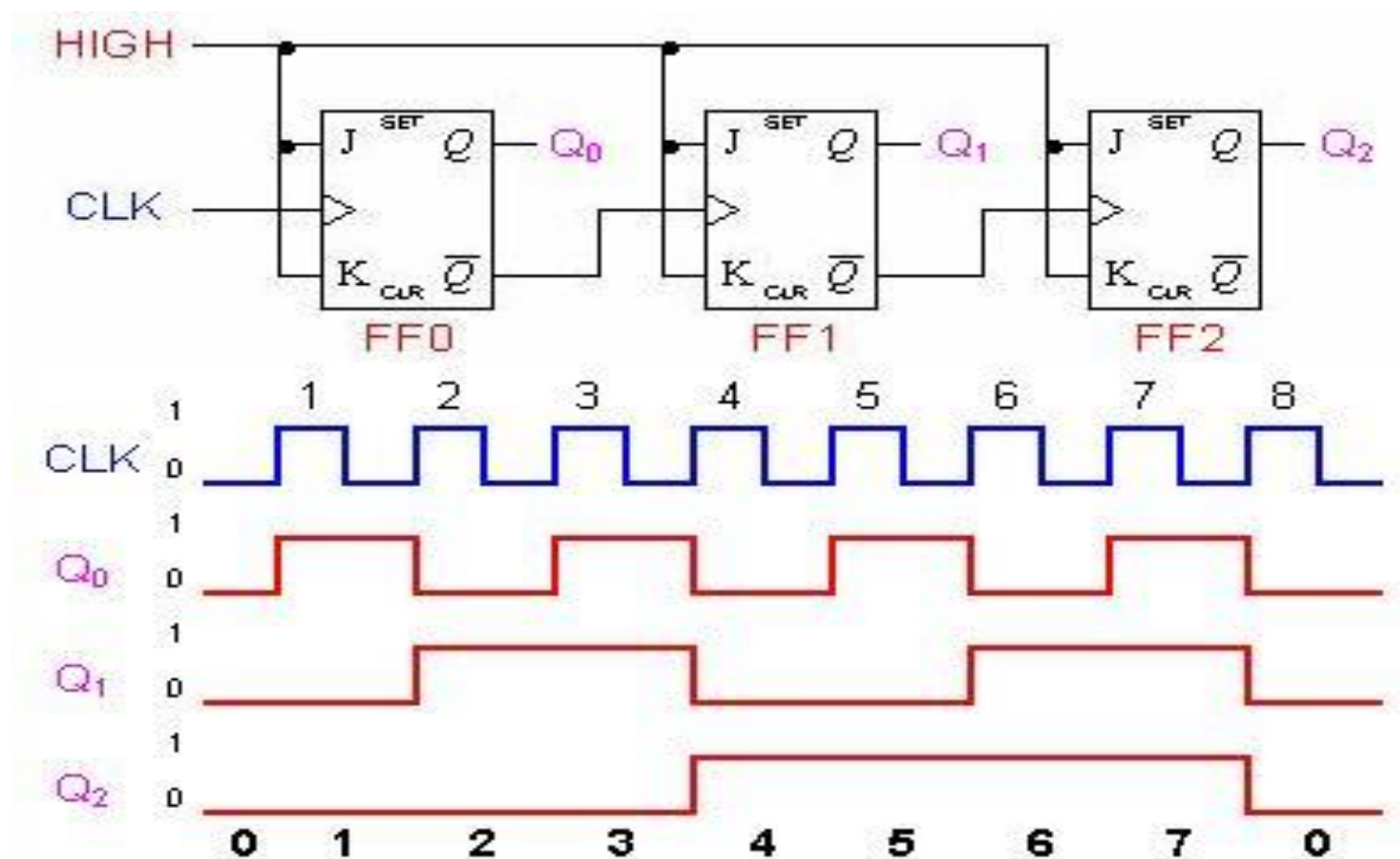

THREE BIT Asynchronous Down COUNTER

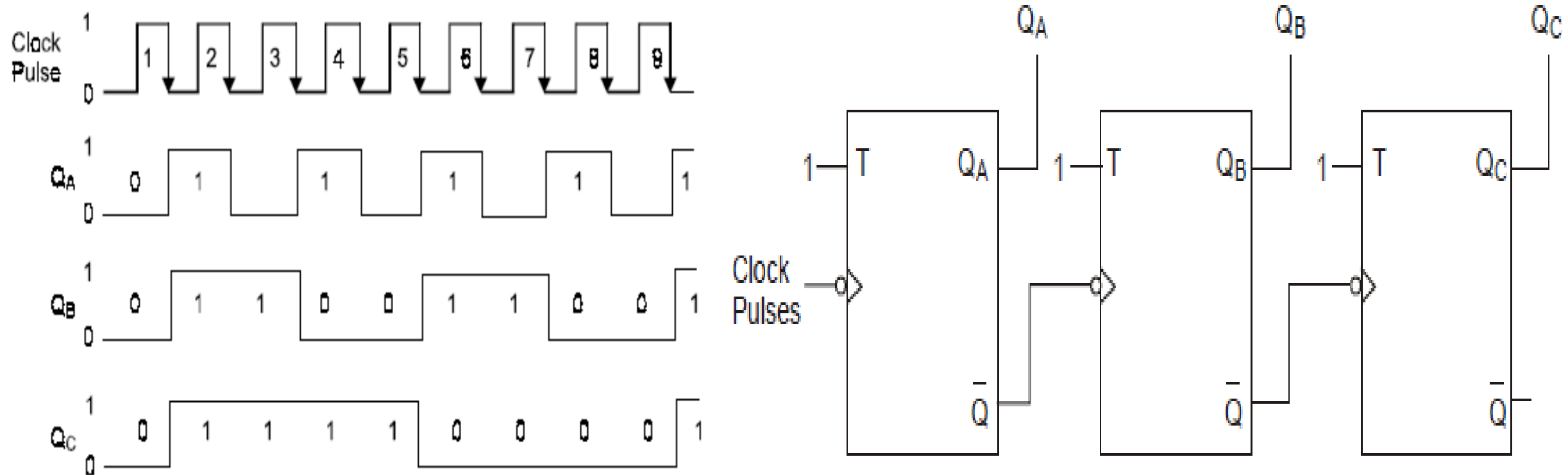

High

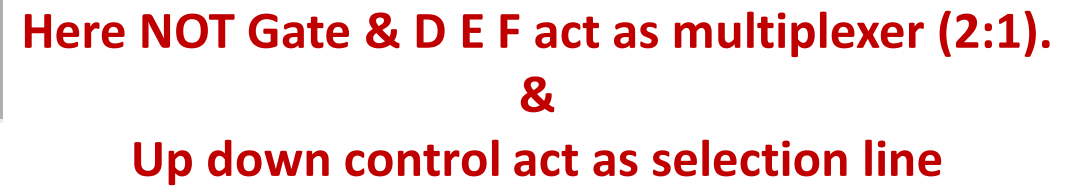


Flip-Flop Pins

- Input Pin (like JK or T or D or SR)
- Clock Pin (+ve or -ve edge trigger)
- Reset pin /Clear Pin (Can Reset Low or High)
- Pre-set Pin


With the help of Pre-set Pin we can force FF to set 1

With the help of Reset function to clear FF to 0

Pre-set and Reset Function

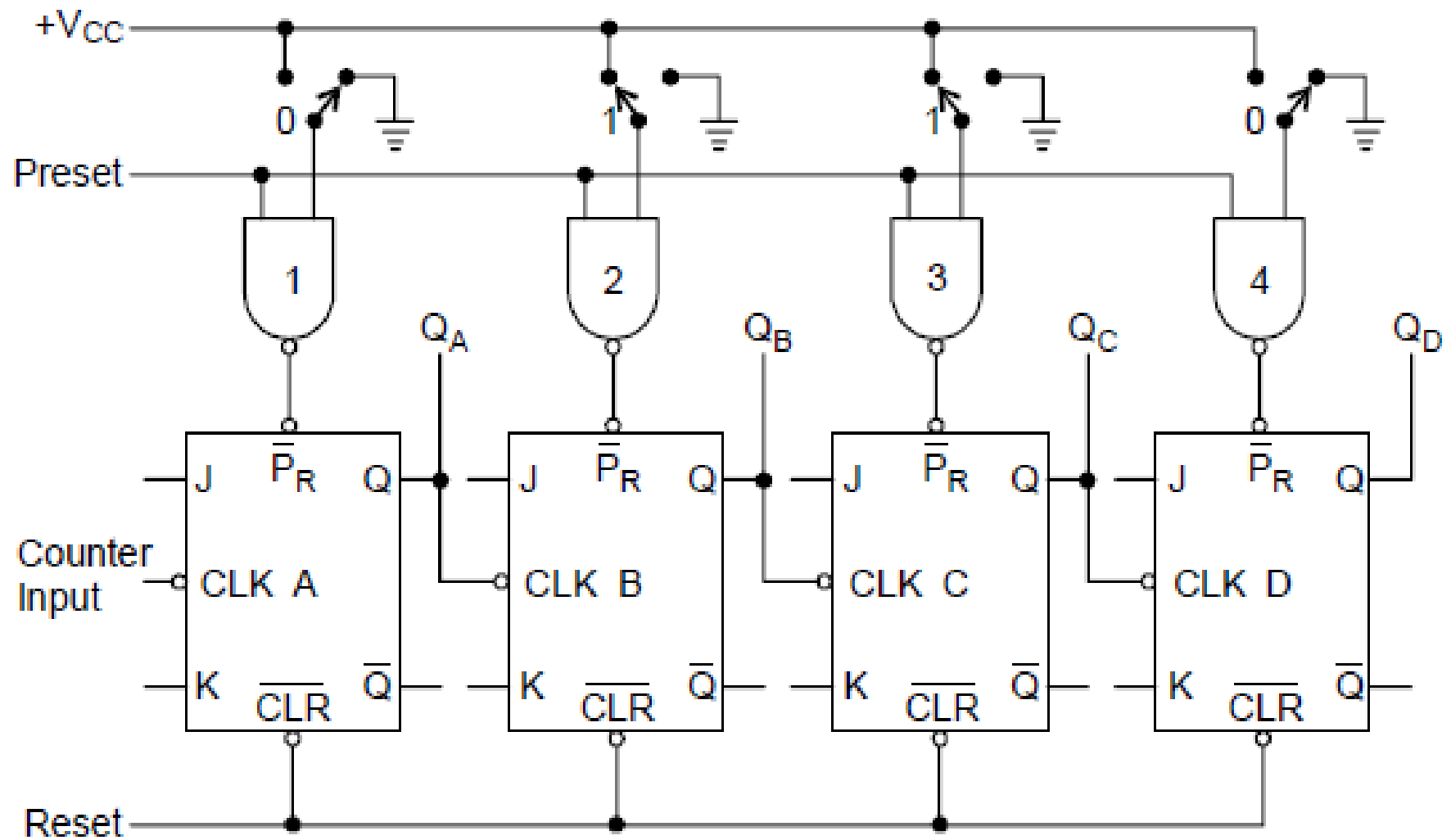

A Decade Counter (asynchronous counter)

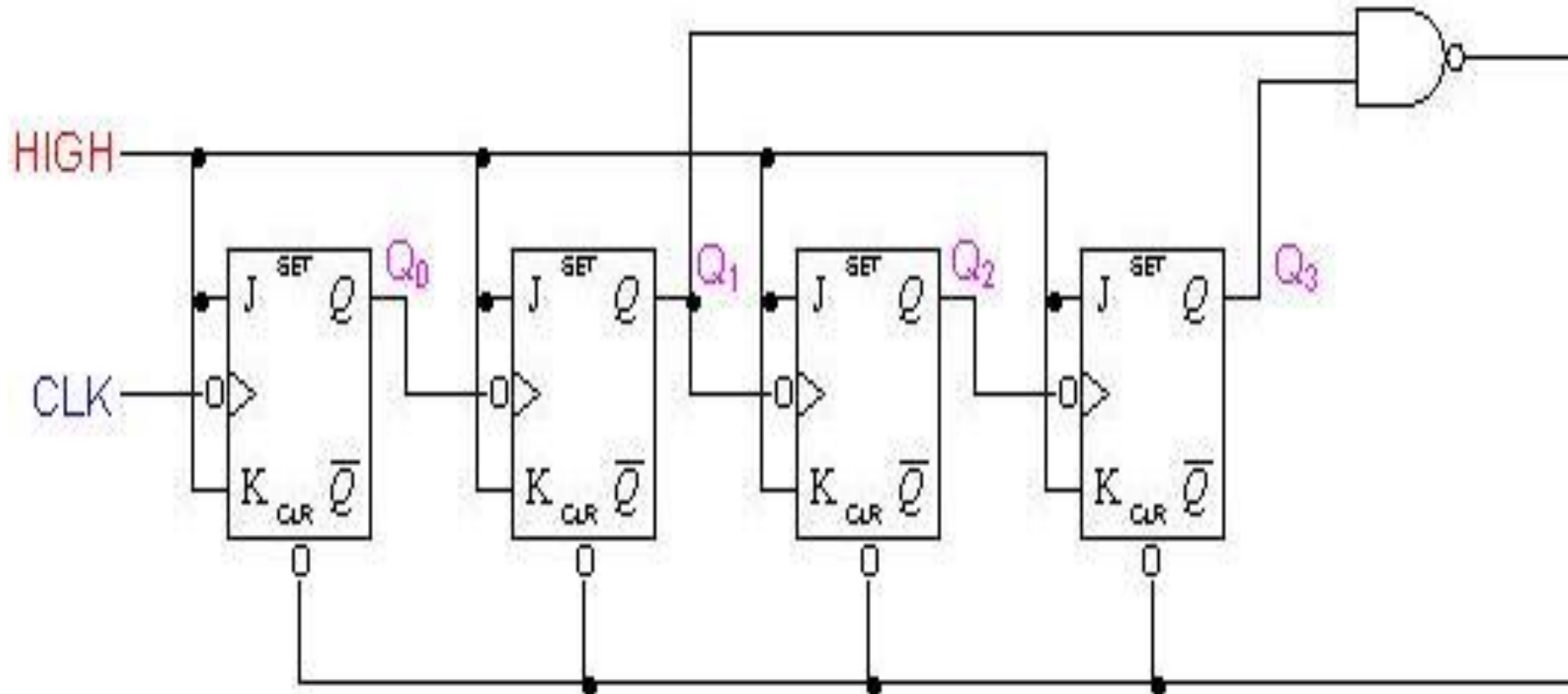

Design a 4 bit Up Down & Up/Down counter

END

NEXT Synchronous Counter