

UNIT 4

Analog and Digital Electronics

Sequential Circuit

Synchronous Counter

Rajeev Pandey
ECE Department

The procedure to design a synchronous counter is listed here.

- Obtain the truth table of the logic sequence for intended counter to be designed. Alternatively obtain the state diagram of the counter.
- Determine the number and type of flip-flop to be used.
- From the excitation table of the flip-flop, determine the next state logic.
- From the output state, use Karnaugh map for simplification to derive the circuit output functions and the flip-flop output functions.
- Draw the logic circuit diagram.

Excitation Table of FFs

Q_t	Q_{t+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Q_t	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1


Figure 9.7: Characteristic table of SR and D flip-flop

Q_t	Q_{t+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q_t	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Synchronous Decade Counter Using JK Flip-Flop

State Diagram

 

Q_t	Q_{t+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Truth Table

Present State				Next State				Output							
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀	J ₃	K ₃	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1

K map for J0 & K0

Q_1Q_0		00	01	11	10
Q_3Q_2	00	1	X	X	1
	01	1	X	X	1
	11	X	X	X	X
	10	1	X	X	X

$$J_0 = 1$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00	X	1	1	X
	01	X	1	1	X
	11	X	X	X	X
	10	X	1	X	X

$$K_0 = 1$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00		1	X	X
	01		1	X	X
	11	X	X	X	X
	10			X	X

$$J_1 = \overline{Q}_3 Q_0$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00	X	X	1	
	01	X	X	1	
	11	X	X	X	X
	10	X	X	X	X

$$K_1 = \overline{Q}_3 Q_0$$

Figure 9.12: Karnaugh maps of J_1 and K_1

Q_1Q_0		00	01	11	10
Q_3Q_2	00			1	
	01	X	X	X	X
	11	X	X	X	X
	10			X	X

$$J_2 = Q_1 Q_0$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00	X	X	X	X
	01			1	
	11	X	X	X	X
	10			X	X


$$K_2 = Q_1 Q_0$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00				
	01			1	
	11	X	X	X	X
	10	X	X	X	X


$$J_3 = Q_3Q_0 + Q_2Q_1Q_0$$

Q_1Q_0		00	01	11	10
Q_3Q_2	00	X	X	X	X
	01	X	X	X	X
	11	X	X	X	X
	10		1	X	X

$$K_3 = Q_3Q_0 + Q_2Q_1Q_0$$

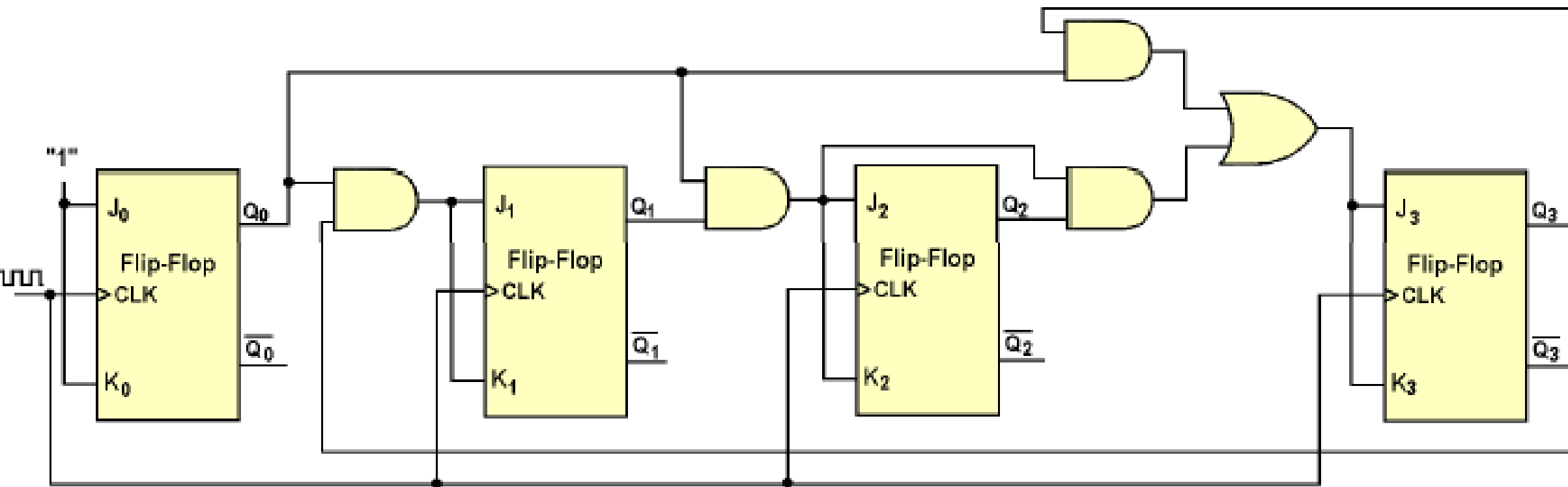

 Design of a Synchronous Modulus-Six Counter Using SR Flip-Flop



Q_t	Q_{t+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

[Present State			Next State			Output					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	R_2	S_2	R_1	S_1	R_0	S_0
0	0	0	0	1	0	0	X	1	0	0	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	1	1	0	1	0	X	0	0	1
1	1	0	1	0	1	X	0	0	1	1	0
1	0	1	0	0	1	0	1	0	X	X	0
0	0	1	0	0	0	0	X	0	X	0	1

Q_1Q_0		00	01	11	10
Q_2	0	0	0	0	1
	1	X	X	X	1

$$R_0 = Q_1 \cdot \overline{Q_0}$$

Q_1Q_0		00	01	11	10
Q_2	0	X	1	1	0
	1	X	0	X	0

$$S_0 = \overline{Q_2} \cdot Q_0$$

Figure 9.19: Karnaugh maps of R_0 and S_0

Q_1Q_0		00	01	11	10
Q_2	0	1	0	X	X
	1	X	0	X	0

$$R_1 = \overline{Q_1} \cdot \overline{Q_0}$$

Q_1Q_0		00	01	11	10
Q_2	0	0	X	0	0
	1	X	X	X	1

$$S_1 = Q_2$$


Figure 9.20: Karnaugh maps of R_1 and S_1

Q_1Q_0		00	01	11	10
Q_2	0	0	0	1	0
	1	X	0	X	X


$$R_2 = Q_1 \cdot Q_0$$

Q_1Q_0		00	01	11	10
Q_2	0	X	X	0	X
	1	X	1	X	0

$$S_2 = \overline{Q_1}$$

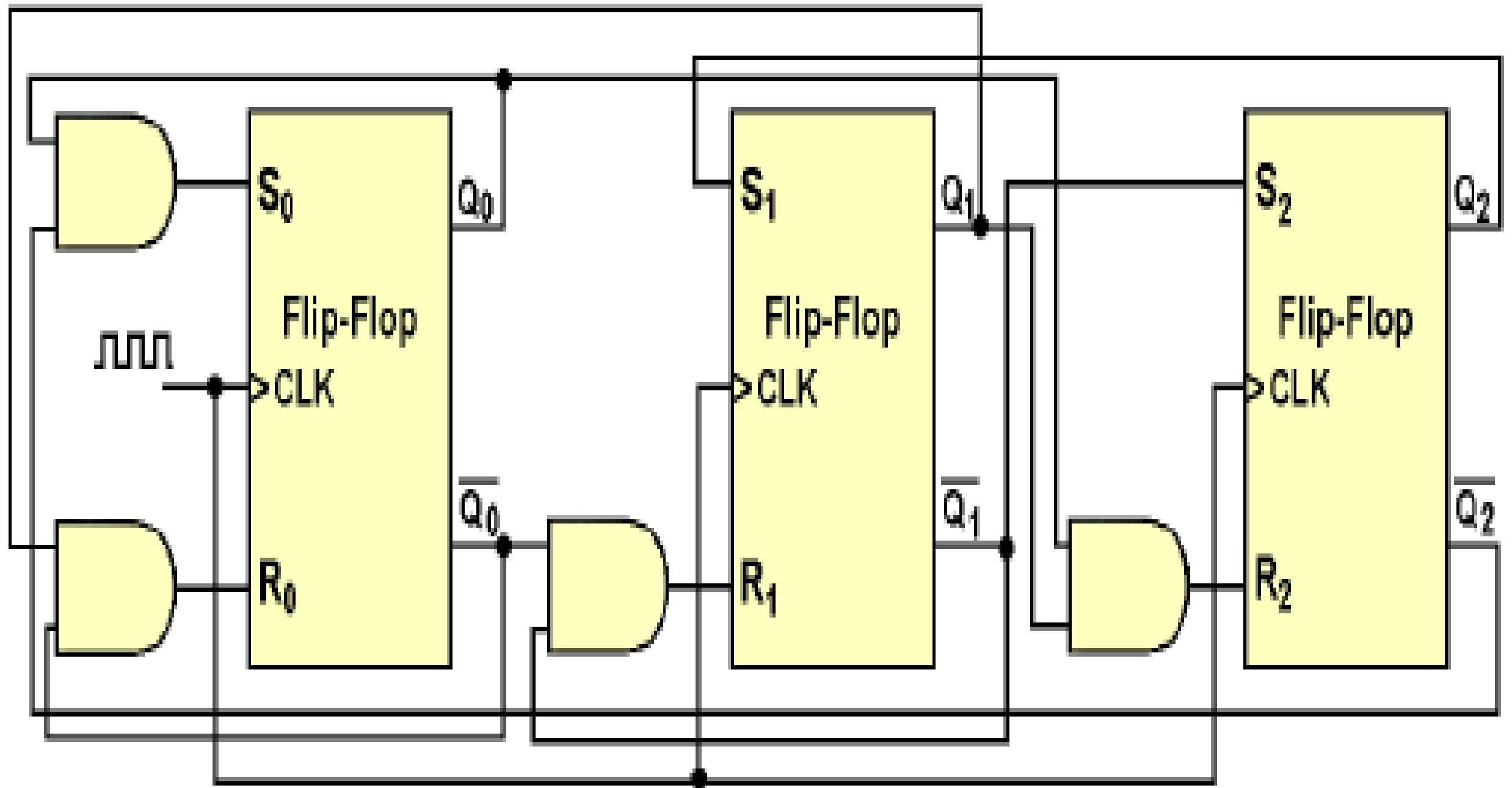

Binary Up-Down Counters using D FF

 

If control input
 $X=0$ counter act as
UP Counter


If the control input
 $X=1$ counter act as
Down counter

X	A	B	A_{n+1}	B_{n+1}	D_A	D_B
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

Q_t	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

$D_B = \bar{B}$

	AB	00	01	11	10
X	0	1	0	0	1
	1	1	0	0	1

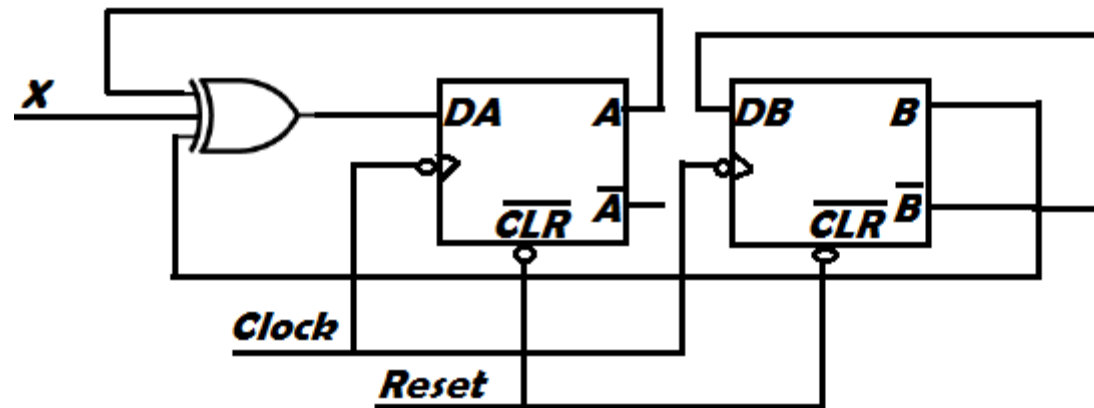


$D_A = \bar{X}(\bar{A}\bar{B} + A\bar{B}) + X(\bar{A}\bar{B} + AB)$
 $= X \oplus A \oplus B$

	AB	00	01	11	10
X	0	0	1	0	1
	1	1	0	1	0

$$D_A = \bar{X}(\bar{A}\bar{B} + A\bar{B}) + X(\bar{A}\bar{B} + AB)$$

$$= X \oplus A \oplus B$$


Johnson counter

 

State	Q_D	Q_C	Q_B	Q_A	Binary equivalent	Output decoding
1	0	0	0	0	0	$\bar{A} \bar{D}$
2	0	0	0	1	1	$A \bar{B}$
3	0	0	1	1	3	$B \bar{C}$
4	0	1	1	1	7	$C \bar{D}$
5	1	1	1	1	15	$A D$
6	1	1	1	0	14	$\bar{A} B$
7	1	1	0	0	12	$\bar{B} C$
8	1	0	0	0	8	$\bar{C} D$

Ring counter

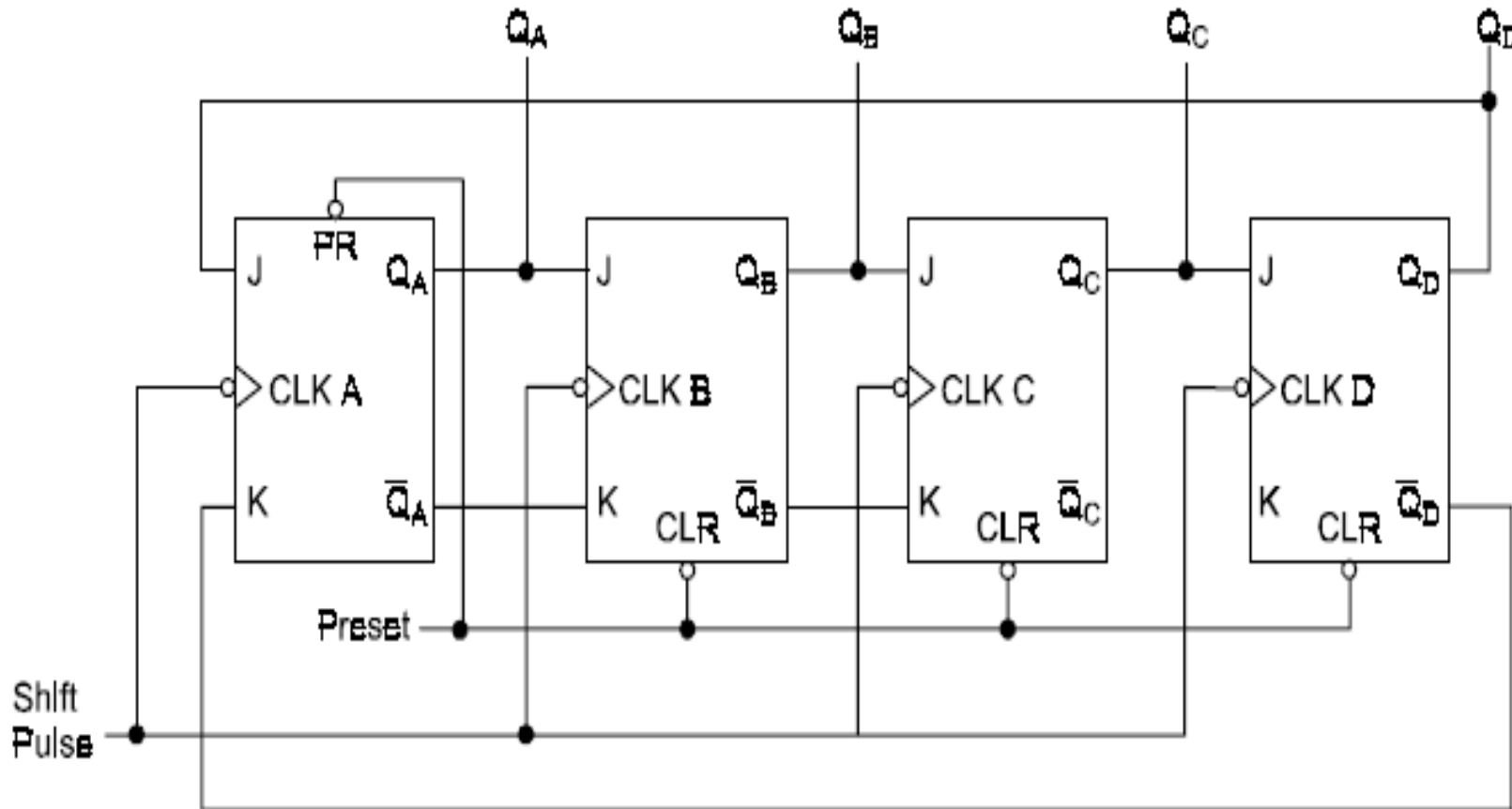Pre-set used to insert 1 in FF A at the same time all the FF reset to 0 then simply act shift register at each clock edge.



<i>States</i>	<i>Counter output</i>			
	Q_A	Q_B	Q_C	Q_D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0

UNIT 4 END