

# UNIT 4

## Analog and Digital Electronics


### Sequential Circuit

### Latches and Flip-Flops

Rajeev Pandey  
ECE Department

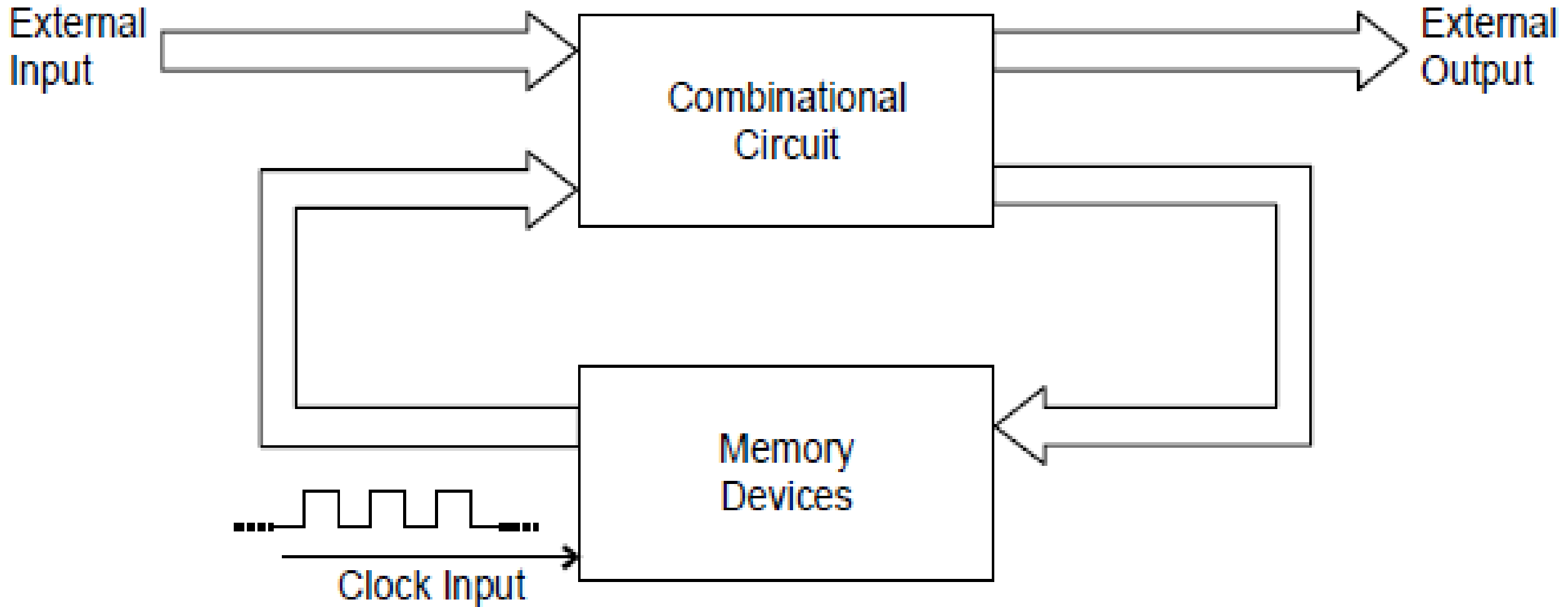
# Sequential Circuit

Sequential circuit are those in which output at any given time not only dependent on the input, present at that time but also on previous output.



 
# NOR Latch (Bistable state)

Nor gate if any one input is '1' output will be '0'.




$S$	$R$	$Q_{n+1}$	$\overline{Q_{n+1}}$	Operation
0	0	$Q_n$	$\overline{Q_n}$	hold
1	0	1	0	set
0	1	0	1	reset
1	1	0	0	not allowed

 

 
# NAND Based SR latch

(In NAND gate if one input is '0' output will be '1'.




$S$	$R$	$Q_{n+1}$	$\overline{Q}_{n+1}$	Operation
0	0	1	1	not allowed
0	1	1	0	set
1	0	0	1	reset
1	1	$Q_n$	$\overline{Q_n}$	hold
 
# Clocked SR Latch(Level Triggered) with active High




S	R	Qn	Qnb	Qn+1	Qn+1b	Comment
0	0	0	1	0	1	Qn (No change)
		1	0	1	0	
0	1	0	1	0	1	Reset
		1	0	0	1	
1	0	0	1	1	0	Set
		1	0	1	0	
1	1	0	1	0	0	indeterminate
		1	0	0	0	

# Clocked NAND SR LATCH Active High


 


(a)


S	R	S'	R'	Q <sub>n</sub>	Q <sub>n</sub> b	Q <sub>n+1</sub>	Q <sub>n+1</sub> b	Comment
0	0	1	1	0	1	1	1	indeterminate
				1	0	1	1	
0	1	1	0	0	1	0	1	Reset
				1	0	0	1	
1	0	0	1	0	1	1	0	Set
				1	0	1	0	
1	1	0	0	0	1	0	1	Q <sub>n</sub> (No change)
				1	0	1	0	

 

# CLOCKED JK Latch NAND Based

  


# Truth Table

 



$J$	$K$	$Q_n$	$\overline{Q}_n$	$S$	$R$	$Q_{n+1}$	$\overline{Q}_{n+1}$	Operation
0	0	0	1	1	1	0	1	<i>hold</i>
		1	0	1	1	1	0	
0	1	0	1	1	1	0	1	<i>reset</i>
		1	0	1	0	0	1	
1	0	0	1	0	1	1	0	<i>set</i>
		1	0	1	1	1	0	
1	1	0	1	0	1	1	0	<i>toggle</i>
		1	0	1	0	0	1	



# JK LATCH NOR BASED

 


# JK as a toggle Switch

  

 
# Master Slave JK FF


- When  $J=K=1$  Toggle
- When the Clock pulse width is high, the output changes or toggle one or more in the same input  $J=K=1$  the same clock period.
- This Problem is known as Race Around Condition.




# Master Slave JK FF NAND Based

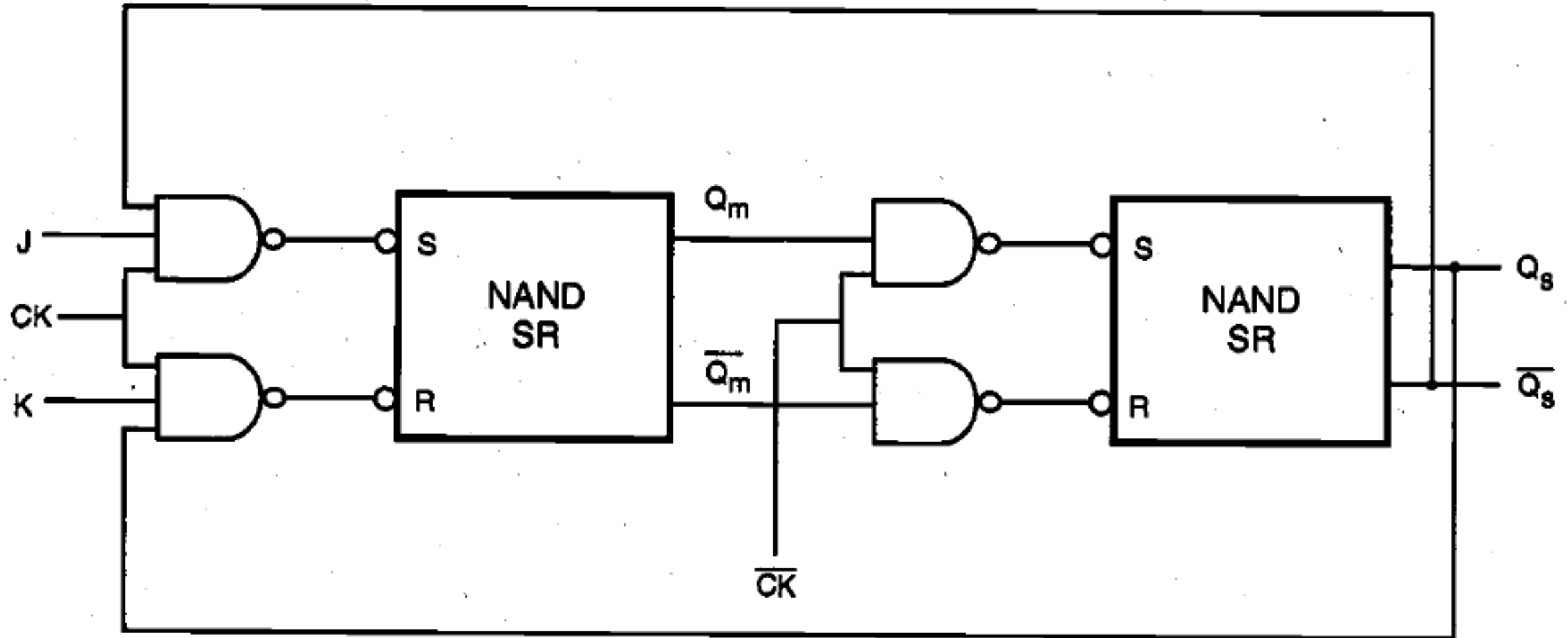


# Master Slave JK FF NOR Based

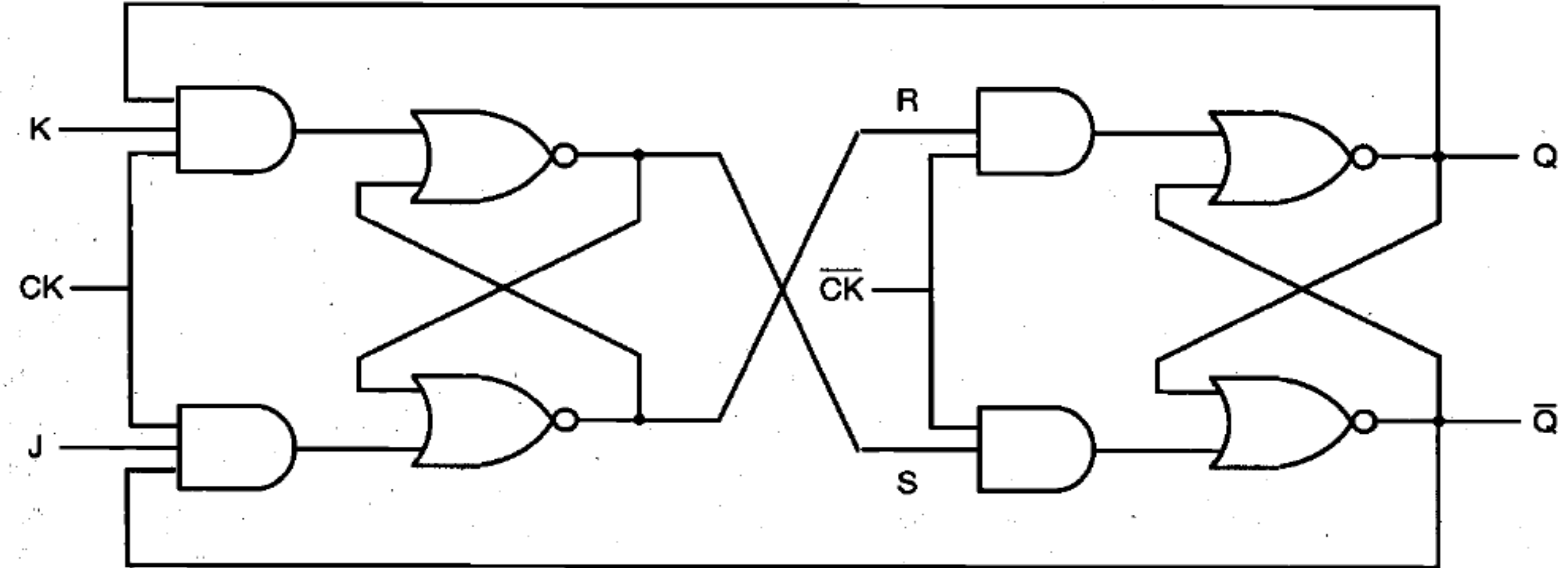

# D Latch

 


D	$Q_{n+1}$
0	0
1	1

 


$$Q_{n+1} = D$$

T FF  $\rightarrow$  Toggle FF

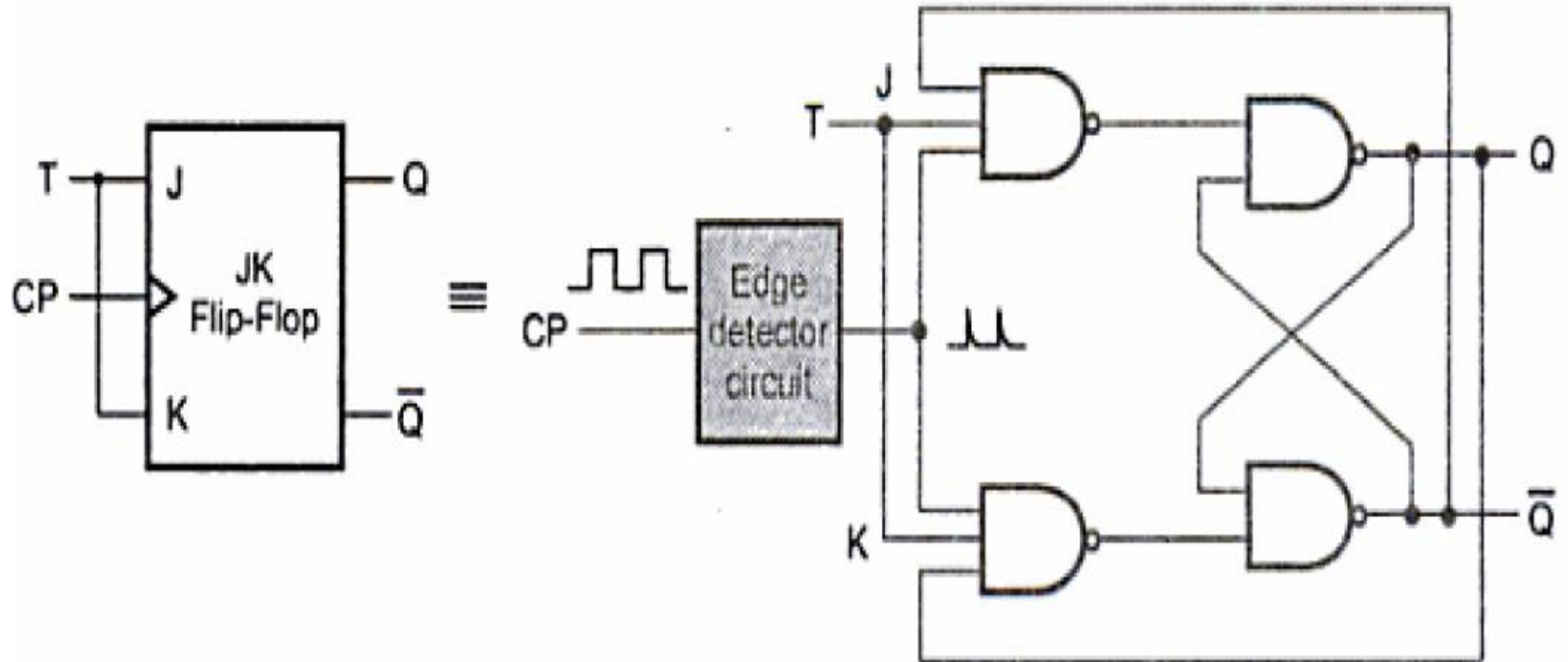

# T Flip-flop

 

(a) Logic symbol


$Q_n$	T	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

b) Truth table

$\equiv$

T	$Q_{n+1}$
0	$Q_n$
1	$\overline{Q_n}$

(c) Characteristic equation

 



# RS FF Truth Table & Excitation Table

R	S	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	*

Table 6.5 (a) RS Truth table

$Q_n$	$Q_{n+1}$	R	S
0	0	X	0
0	1	0	1
1	0	1	0
1	1	0	X

Table 6.5 (b) RS Excitation table

**Find  $Q_{n+1}$  Expression**

# JK FF Truth & Excitation Table

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$

Table 6.6 (a) JK truth table

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



Table 6.6 (b) JK excitation table

$$Q_{n+1} = J Q_n + K \overline{Q_n}$$

# Flip-Flop Conversion




## SR FF To D FF

Input	Present state	Next state	Flip-flop inputs	
D	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

  


# JK To D FF

Input	Present state	Next state	Flip-flop inputs	
D	$Q_n$	$Q_{n+1}$	J	K
0	0	0	0	X
0	1	0	X	1
1	0	1	1	X
1	1	1	X	0

   

Analysis

 Prove that the given circuit is equivalent To T FF



END

NEXT is Shift Registers And Counters